

Time : 3 Hrs.

**Note :**

1. Part 'A' may be attempted in first 5 pages of Answer Sheet.  
भाग 'क' के सभी उत्तर, उत्तर-पुस्तिका के प्रथम पांच पृष्ठों में ही करने हैं।
2. Part 'B' in rest of the Sheets of Answer Sheet.  
भाग 'ख' के उत्तर, उत्तर-पुस्तिका के अगले शेष पृष्ठों में लिखिये।
3. Answers may be given in English or Hindi.  
प्रश्नों के उत्तर अंग्रेजी अथवा हिन्दी में दीजिये।

**Part 'A'**

## 1. Attempt any ten questions:

10x2= 20 - 18↑

- (i) Convert  $(111)_2$  into decimal number.
- (ii) Write base of binary number.
- (iii) Convert  $(56B)_{16}$  into octal number.
- (iv) What do you mean by alpha numeric code?
- (v) Define negative logic.
- (vi) RTL stand for .....
- (vii) Define reflected code.
- (viii) DCL stand for .....
- (ix) Write name of basic gates.
- (x) What do you mean by edge triggered flip flop?
- (xi) Write disadvantages of combinational logic circuits.
- (xii) Write advantages of K-map technique.
- (xiii) Define register.
- (xiv) Write types of A/D convertors.

$$\overline{A} \cdot \overline{B} \cdot \overline{C} + BC + AC$$

+ c (ABC)

0101 0110 1011

2 5 3

PagalEngineer.com

$$\begin{array}{r} 16 \\ 16 \\ 16 \\ \hline 256 \end{array}$$

$$\begin{array}{r} 16 \\ 16 \\ 16 \\ \hline 256 \end{array}$$

$$\begin{array}{r} 64 \\ 64 \\ 64 \\ \hline 192 \end{array}$$

$$\begin{array}{r} 1024 \\ 320 \\ 90 \\ \hline 1394 \end{array}$$

$$\begin{array}{r} 256 \\ 256 \\ \hline 512 \end{array}$$

$$\begin{array}{r} 1024 \\ 256 \\ \hline 1280 \end{array}$$

$$\begin{array}{r} 1280 \\ 96 \\ \hline 1376 \end{array}$$

## 2. Attempt any 5 of the following questions:

- (i) Design OR gate with help of NAND gates.
- (ii) Simplify  $\overline{A} \cdot \overline{B} \cdot \overline{C} + BC + AC$
- (iii) Discuss error detection code with its applications.
- (iv) Explain K-map technique for minimization of a logic operation.

$$\overline{A} \cdot \overline{A} \cdot \overline{B} \cdot \overline{B}$$

5 x 4 = 20

- (v) Perform addition of two unsigned numbers with example.
- (vi) Convert  $(DAB)_{16}$  into octal and binary numbers.
- (vii) Design a half subtractor and write its truth table.
- (viii) Write various applications of A/D converters.

## PART-B

Attempt any 3 of the following questions:

3 x 20 = 60

- 95 ↑

- 3. (a) Explain the working of SR flip-flop also write its truth table.  
(b) Design a full adder circuit and explain its working.
- 4. (a) Simplify the following expression using K-map :  
 $f(A, B, C, D) = \sum(0, 1, 3, 5, 9, 11, 13, 15)$   
(b) Design a 3 bit synchronous counter and explain its working.
- 5. (a) Explain the working of TTL logic family with help of neat circuit diagram.  
(b) Design 1 x 8 demultiplexer and explain its functioning.
- 6. (a) Explain the working of CMOS logic family with help of neat circuit diagram.  
(b) Design a 8 bit down counter.
- 7. (a) Explain the working of a parallel in parallel out shift register.  
(b) Explain working of any one type of D/A converter with neat diagram.