

Basic Electricity

3K4-IA-04

Time : 03 hrs.]

[M.M. : 100

Note :—

1. Part 'A' may be attempted in first 6 pages of Answer Sheet.
भाग 'क' के सभी उत्तर, उत्तर-पुस्तिका के प्रथम छः पृष्ठों में ही करने हैं।
2. Part 'B' in rest of the Sheets of Answer Sheet.
भाग 'ख' के उत्तर, उत्तर-पुस्तिका के अगले शेष पृष्ठों में लिखिये।
3. Answers may be given in English or Hindi.
प्रश्नों के उत्तर अंग्रेजी अथवा हिन्दी में दीजिये।

PART – A**1. Attempt any ten questions :****(10x2=20)**

- (a) The resistance of 200W, 200V lamp is
- (b) Specific resistance is measured in
- (c) State maximum power transfer theorem.
- (d) What is principle of self and mutual induction.
- (e) Explain Len's law.
- (f) Define Power
- (g) Define Energy.
- (h) Define Gauss's Theorem.
- (i) What is Electrical intensity and Electrical field ?
- (j) Differentiate between AC and DC.
- (k) State Nortons Theorem
- (l) Write formulae for stored in an inductor and in capacitor
- (m) Define power factor.
- (n) Write methods of producing deflecting torque.

2. Attempt any five questions :

- Explain repulsive type moving iron instrument ?
- Explain principle and working of dynamometer type MI instruments ?
- Draw a sinusoidal waveform and write its equation along with meaning of all symbols.
- Explain how energy stored in a magnetic field.
- Explain the application of Thevenin's Theorem and Norton's theorem in DC circuit.
- Convert the star circuit in Fig. 1 into its equivalent delta circuit.

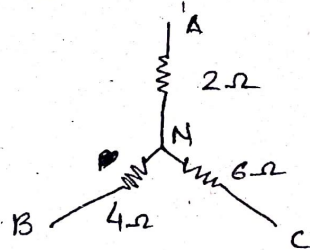


Fig. 1

- Define peak value and time period of the alternating quantity.
- Derive the condition for resonance in a series a.c. circuit.

PART- B

Attempt any three questions :

(3x20=60)

- An alternating voltage is given by $V = 141.4 \sin 314 t$. Find
(i) Frequency (ii) R.M.S. value (iii) Average value (iv) Instantaneous value of voltage when t is 3 m sec
 - Determine the value of Resistance 'R' as shown in Figure 2 using KVL and KCL.

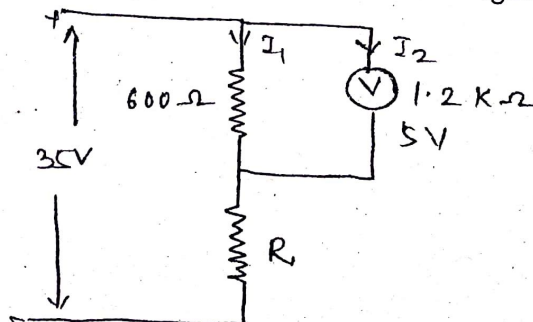


Fig. 2

- Explain in details PMMC instrument with the help of neat diagram.
 - Define (i) Faraday's Law (ii) Permeability (iii) Reluctance (iv) Hysteresis
- Explain superposition theorem with an example.
 - Explain current source and voltage source and give one example of each.
- Derive the analogy between electric and magnetic circuits.
 - Explain Hysteresis loop and also derive relation between B & H.
- With the help of neat diagram, explain the construction and operation of an induction type instruments ?
 - How ammeter and voltmeter can be constructed using PMMC instruments.